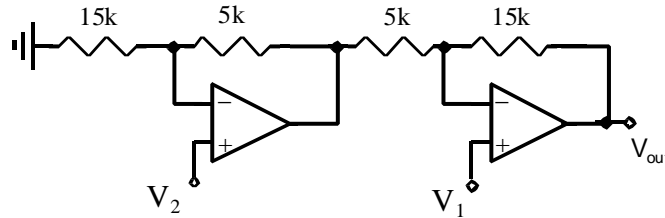


ANALOG & DIGITAL ELECTRONICS


HOMEWORK ASSIGNMENT 7: Due Friday, April 13.

1. Consider the op amp circuit below. Find the output as a function of the inputs.




2. Consider the circuit at the right.

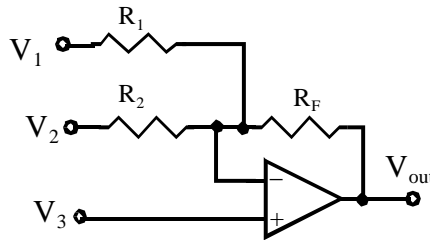- a) Find the output voltage, V_o , in terms of the resistors R_1 , R_2 , and R_F ; and the three input voltages, V_1 , V_2 , and V_3 .
- b) Find the numerical value of V_o if $R_1 = 5k$, $R_2 = 10k$, $R_F = 20k$, $V_1 = 2V$, $V_2 = 1V$, and $V_3 = 2.5V$.



3. You have a device that produces an output voltage that depends linearly on the temperature, however the output at $0^\circ\text{C} = 200\text{mV}$ and the output at $100^\circ\text{C} = 400\text{mV}$. Design a single op amp circuit that will take the voltage produced by this device and produce an output voltage of 0V at 0°C and 1.00V at 100°C . You may use a fixed reference voltage of either 1.00V or -1.00V in your circuit if you need to.
4. Design a simple band pass filter using a single op amp, the one that looks like two cascaded RC filters. The cutoff frequency of the low pass part should be $20,000\text{ Hz}$ and the cutoff of the high pass should be $5,000\text{ Hz}$. The circuit should have a gain of -8 at $10,000\text{ Hz}$.

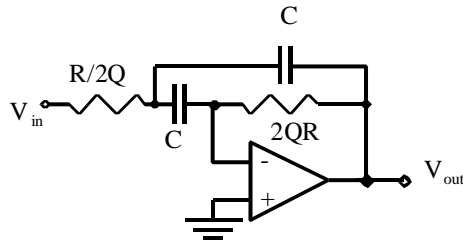5. Consider the single amp band pass filter you will use in the laboratory. Choose values to give a $Q = 4$ and a center frequency (resonant frequency) of $40,000\text{ Hz}$. What is the gain at the center or resonant frequency?



6. Design a second order low pass filter with a damping of 0.5 and a "cutoff" or "resonant frequency of 16 kHz . Use a Sallen Key equal component value filter. Use an $R \geq 20k\Omega$. (See below for the reason.)
7. Convert the above Sallen Key filter into a third order filter by adding a RC stage in front of the Sallen Key filter. Choose the cutoff of this stage at 16 kHz . Choose the component values so the two filters will not interact.